



DSP Integrated Circuits

Chapter 6: DSP H/W Design

Prof. Jaeseok Kim

Communication SoC Design Lab.

Yonsei University

Contents

- ◇ H/W Key Components for DSP design
- ◇ Analog I/O





H/W Key Components

H/W Key Components (1)

- ◇ Multiplier
- ◇ Multiplier-Accumulator (MAC)
- ◇ Arithmetic Logic Unit (ALU)
- ◇ Shifter
- ◇ Address Generator (AG)
- ◇ Program Sequencer (PS)
- ◇ Memory Architecture



H/W Key Components (2)

◇ Multiplier (1)

■ Desirable Features

- Speed : comparable to RAM access time; fully parallel operation
- Input Formats : 2's complement or unsigned, fractional or integer
- Mixed mode : Signed or unsigned—a desirable enhancement
- ⊗ Output Formats : Right-shifted (“Integer”) or left-shifted (“Fractional”)
- ⊗ Extended or double-precision option
- ⊗ Fixed point vs. floating-point tradeoffs
- ⊗ Single-cycle multiply of two inputs X and Y; bussing, pipelining issues
- Input and output registers configurable for latching (pipelined operation) or transparency (minimum latency)




H/W Key Components (3)

◆ Multiplier (2)

■ Bit and Word Formats

 1) The Extra Bit in 2's complement multiplication




H/W Key Components (4)

◆ Multiplier (3)

■ Bit and Word Formats

2) Sign control and mixed mode

 

X	Y	Result
Signed	Signed	Signed
Unsigned	Unsigned	Unsigned
Signed	Unsigned	Signed (mixed-mode)
Unsigned	Signed	Signed (mixed-mode)

H/W Key Components (5)

◆ Multiplier (4)

■ Bit and Word Formats

3) Rounding Issues

MSH	LSH	
10011011	10101010	Full-width output, $LSH > FS/2$
	+ 10000000	Augment LSH, then truncate →
= 10011100		Rounded output incremented
10011011	00101010	Full-width output, $LSH < FS/2$
	+ 10000000	Augment LSH, then truncate →
= 10011011		Rounded output unchanged

■ Speed, accuracy, cost tradeoffs

■ Pipelined multipliers

● Without pipelining

- One-cycle output delay, Low frequency

● With pipelining

- Multiple output delay, High frequency

H/W Key Components (6)

◇ Multiplier-Accumulator (MAC) (1)

■ Desirable Features



- ⊕ Single-cycle multiply-accumulate
- Adequate guard bits (extension bits) in the accumulator (ACC)
- Overflow detection before it occurs
- ⊕ Unbiased Rounding
- ⊕ Saturation Arithmetic
- ⊕ Internal feedback paths to lessen overhead on loops, speeding computation common DSP “primitives”
- ⊕ User beware : distinguish throughput (best-case, pipeline full) from latency single-time operation)



H/W Key Components (7)

◆ MAC (2)

  ■ Pipelined multiplier with transparent option




H/W Key Components (8)

◇ MAC (3)

- Width Issues and overflow dynamic range

The Feedback path C provides the accumulator action :

$$R(n+1) = X(n+1) * Y(n+1) \pm R(n)$$

 

H/W Key Components (9)


◇ MAC (4)

■ Output structure, overflow, rounding control and saturation Logic

- The extra-width output to be saturated, brought back to data-bus width, and/or transmitted in MSW and LSW
- Rounding is essential MAC option, but highest accuracy is attained by avoiding rounding

* MSW (Most-Significant Word)

* LSW (Lest-Significant Word)

 


b. Elements of the enhanced MAC structure of the ADSP-1101 Integer Arithmetic Unit.

H/W Key Components (10)

◇ MAC (5)

■ Extra registers and feedback paths

 - ✚ Expanded computing power results from extra intermediate registers and feed back paths



H/W Key Components (11)

◇ Arithmetic Logic Unit (ALU) (1)

■ Desirable Features

- Adequate accuracy and chainability for high-precision computation
- Arithmetic Functions : add, subtract, add with carry, subtract with borrow, absolute value
- Logic flags : zero, equal, less than, greater than, carry ...
- Divide and (less important) multiply capability
- Efficient data movement and computation :
 - Data moves plus arithmetic in same cycle
 - Two operands loadable into the ALU on each cycle
- Adequate Register Files :
 - Dual-set for context switching (for storing data during interrupts)
or: Register File for fast access and storage of intermediate results
- Conditional operations, e.g., add + (Shift if Flag Set) are an asset

H/W Key Components (12)

◇ ALU (2)

■ Desirable Features

- Conditional operations, e.g., add + (Shift if Flag Set) are an asset
- Adequate Feedback pathways : Output to input (accumulate); and, if linked to shifter, ALU inputs to shifter or shifter inputs to ALU
- Pipeline or transparent flow through option on input registers
- Close association with Shifter for scaling operations common in DSP
- Double-precision capability with minimum lost time



H/W Key Components (13)

◇ ALU (3)

■ ALU Functions and Data Formats

■ Condition Flags

- As with a general-purpose ALU, the DSP ALU must signal status information on the computation just performed

■ Rounding

■ Division Capability

- Division occurs in many DSP systems, e.g., predictive coding of speech
- Since division is not among basic MPY or MAC operations, it is a key LAU primitive operation

■ Saturation Logic

■ Arithmetic Plus Conditional Shift


- ALU can conditionally shift its result up or down during the same cycle, depending on the state of an input flag

H/W Key Components (14)

◇ ALU (4)

■ ALU Architecture Issues

 - Word Width and Easy Paralleling
- Single Cycle Data-Moves-plus-Arithmetic
- Adequate Register Set



- Flexible Internal Data Paths and I/O Pathways

H/W Key Components (15)

◇ Shifter (1)

■ Shifter Definition and Functions

- ⊕ A shifter scales numbers to prevent underflows and overflows and performs conversions between fixed-and floating point
- Unlike the bit-per-cycle shift of general-purpose microprocessors, the DSP shifter must be capable of shifting a word by many bits in a single machine-cycle to preserve single-cycle computation speed

■ Basic Shifter Operations

- N-bit arithmetic and logical shifts (shift-immediate)
- Word rotations and word merges
- Bit-test/bit-set/bit-clear




H/W Key Components (16)

◇ Shifter (2)

■ Shifter Scaling Functions

■ Enhancements for Scaling : provide low-overhead exponent handling

 - Exponent detector
: Uses a priority encoder to translate the number of identical leading bits into a binary number representing the number's base-2 exponent



a. Block diagram.

H/W Key Components (17)


◇ Shifter (3)

■ Shifter Scaling Functions


- Enhancements for Scaling : provide low-overhead exponent handling

- Normalization

 : Fixed-to-floating point conversion, generating a mantissa and an exponent



 - Denormalization : The inverse of normalizat



- Block Floating-Point : derives the exponent of the largest member of a data array

- Block floating-point exponents are determined by exponent-detection logic

H/W Key Components (18)

◇ Address Generator (AG) (1)

■ Desirable Features


- ⊕ Send a precomputed address to data memory
 - Data-array scanning : An AG with its own ALU makes possible it
- Modify the address by a computed offset value
- ⊕ Perform logical (AND, OR, XOR) operations and shifts
- ⊕ Compare a pointer to a preset value (circular buffer)
- ⊕ Reset pointer to buffer origin when pointer = preset
- ⊕ Reset to origin when pointer $\geq$ or $\leq$ preset
- Reverse the order of the bits



H/W Key Components (19)

◇ AG (2)

 ■ General scheme of Data Address Generator (DAG)



$Y = R$; modify R contents
by a computed offset value

H/W Key Components (20)

◇ AG (3)

■ Address Generator Enhancements

● Shift Capability

- Provides simple FFT twiddle-table or butterfly data-pair addressing

● Bit-Reversal Capability

- Either the input is supplied with addresses in bit-reversed order or the output spectrum is returned addressed in bit-reversed order

● Logic Function and Masking Capability

- In table lookups, DAG capability to perform logical operations permits the partial masking of an address field to address a stored function value (more significant half)

● Word-Slice Address Generator

- Replaces AGs implemented with several Bit-Slice ALU
- Programmable, and more flexible solution than fixed-purpose AG chips

● Flexible Modulus Arithmetic

$$R = B + (R - B + M) \text{ MOD } (L)$$


R : the DAG address-register content
B : a base address
M : a computed offset increment
L : the length of the buffer (modulus)

H/W Key Components (21)

◇ Program Sequencer (PS) (1)

■ Sequencer Definition

 - Generates the instruction addresses which determine program flow



a. Instruction sequencer and its relationship to other DSP system components.

H/W Key Components (22)

◇ PS (2)

■ Sequencer Functions

- ⊕ Handle normal program flow, incrementing the program counter by 1 each cycle
- Keep track of subroutine addressing, and manage the return-address stack
- ⊕ Manage loops in an overhead-free manner, controlled by on-chip loop counters
- ⊕ Jump to appropriate exception-handler routines when a data overflow is detected or data rescaling is required
- ⊕ Service interrupts from external I/O devices, jumping to appropriate interrupt service routines and returning to the previous task when done



H/W Key Components (23)

◇ PS (3)

■ Desirable Features : includes the following components

- Program Counter (PC)
- Conditional Logic Tester
- Stack for :
 - Subroutine and Interrupt return addresses
 - Counter values
 - Jump addresses
- Loop Counters

■ Basic Sequencer Requirements

- Adequate Stack Size
- Branch Conditions and Interrupt Prioritization
- Sequencer Pipelining Is Not Recommended
- Forcing a Direct Instruction Address

■ Desirable Sequencer Enhancements

- Stack Boundary Settability
- Zero-Overhead Conditional Branch Capability

H/W Key Components (24)

◇ Memory Architecture (1)

■ Desirable Features DSP Memory

- Separate memory chips to be addressed by DSP components must match their speed
- ⊕ Dual-ported memory has two separate ports, controls, address, and I/O lines, to permit independent accessing
- ⊕ Register files are another way of increasing memory productively without decreasing speed or adding complexity
- FIFO registers act as pipelines to match slower memory to faster processors
- ⊕ Cache memory : the most recently used instructions remain resident
- ⊕ Address generators lessen the demands on memory

$$t(\text{data}) = t(\text{addr. gen.}) + t(\text{data fetch})$$




H/W Key Components (25)

◇ Memory Architecture (2)

■ Von Neumann architecture

 - A single set of address and data lines
 - Both program instructions and data are stored in the single memory
- Common among non-DSP processors
- Strength
 - Low-cost
- Weakness
 - The processor can make one access to memory during each instruction cycle



H/W Key Components (26)

◇ Memory Architecture (3)

■ Harvard architecture

- ⊕ Two independent memory banks and two independent sets of buses (address and data)

- Original

- One bank for inst. One bank for data


- Modified

- One bank for inst. And data, one bank for data

- Two memory accesses per instruction cycle

- More powerful derivatives

 - One program bank and two data banks
- A shortage by one bank can be overcome by module addressing






Analog I/O

Analog I/O

- ◇ Analog-to-Digital Conversion
- ◇ Automatic Gain Control (AGC)
- ◇ Digital-to-Analog Conversion




Analog I/O in DSP System

 


Analog-to-Digital Converter

◆ Successive Approximation A/D Converter

 

Analog-to-Digital Converter

Flash A/D Converter

 

Comparison

Type	Needs S/H?	Cycles /conversion	Advantages	Example
Successive Approximation	Yes	b (for b-bits output)	cheap	8-bit 500KHz 16-bit 400KHz
Flash	No	1	fast	6-bit 400MHz 10-bit 75MHz



Digital-to-Analog Converter

◇ Voltage-scaling D/A Converter


 


Figure 10.2-2 Alternate realization of Fig. 10.2-1 (a).

Digital-to-Analog Converter

◇ Charge-scaling D/A Converter

 

$$v_{OUT} = [b_1 2^{-1} + b_2 2^{-2} + b_3 2^{-3} + \dots + b_N 2^{-N}] V_{REF}$$

Digital-to-Analog Converter

- ◇ Combination of voltage-scaling and charge-scaling


 


Figure 10.2-6 A D/A converter using a combination of voltage-scaling and charge-scaling techniques. The 4 MSBs are accomplished by voltage-scaling and the 8 LSBs are accomplished by charge-scaling.

Automatic-Gain-Control (AGC)

◇ Typical Set-Top Box Demodulator

 

A/D Converter Example



Dual 8-Bit, 60 MSPS A/D Converter

AD9059


FEATURES

- Dual 8-Bit ADCs on a Single Chip
- Low Power: 400 mW Typical
- On-Chip +2.5 V Reference and T/Hs
- 1 V p-p Analog Input Range
- Single +5 V Supply Operation
- +5 V or +3 V Logic Interface
- 120 MHz Analog Bandwidth
- Power-Down Mode: < 12 mW


APPLICATIONS

- Digital Communications (QAM Demodulators)
- RGB & YC/Composite Video Processing
- Digital Data Storage Read Channels
- Medical Imaging


FUNCTIONAL BLOCK DIAGRAM

 

Analog-to-Digital Mapping

 


AGC Example

 




Output from AGC (PWM)

- ◇ Signal Adequate

 



- ◇ Signal too Small

 


- ◇ Signal too Large



Digital-to-Analog Converter

  

Digital-to-Analog Converter

 


Sinx/x Compensation


- ◇ Compensation Filter Included in DAC
 - inverse sinc (sinc^{-1}) filter
 - $x/\sin(x)$
- ◇ Pre-compensating Digital Filter Prior to DAC
- ◇ Stand-Alone Analog Filter after DAC
- ◇ Increase the Sampling Rate



Up-Sampling before DAC

 

Up-Sampling before DAC

 



DSP Integrated Circuits

Chapter 7: Development Tools

Prof. Jaeseok Kim

Communication SoC Design Lab.

Yonsei University

Development Tools

◇ Software tools

- Assemblers, linkers, simulators, debuggers, compilers, code libraries and real-time operating systems

◇ Hardware tools

- Development boards and emulators

◇ Higher-level tools

- Block-diagram based code generation environments



Software tools(1)

◇ Assemblers

- Assemblers translate assembly-language mnemonics into binary object code
- Assembler statements must be adequate to
 - Specify the structure of programs
 - Declare variables
 - Identify where referenced variables and I/O ports will reside the target

◇ Linkers

- Linkers couples together relocatable object modules prepared by the assembler, including library subroutines
- Produces absolute memory images for run-time execution



Software tools(2)

◇ Simulators

- The simulator permits programs to be fine-tuned in software prior to making the significant effort to bring up the target system in hardware

◇ Debuggers

- Front-end program that provides the user interface for an emulator or simulator
- Key features
 - Data display and editing
 - Symbolic and source-level debugging
 - Single-stepping
 - Breakpoints



Hardware tools

◇ The PROM splitter

- The PROM splitter performs the function for target physical memory chips
- Chunks of code destined for ROM are divided up into sizes that fit into regions of physical memory chips


◇ Target emulation

- Emulator: A real-time debug tool that takes over where the simulator leaves off
- External hardware and software allow monitoring and controlling of the processor in the target system



Higher-level tools

 - ◆ Block-diagram based code generation environments
 - SPW, Matlab simulink, Systemview



Design flow

