

CT500 PCB Application Note

Version 1.0

Shmt Co., Ltd.



REVISION HISTORY PAGE

Issue	Rev No.	Originator	Details of Change	Date
1	1.0	EAST	Initial Version	2007-06-13
2				
3				
4				
5				

Confidential

Technical documents for Firmware

Copyright © 2007 Shmt Limited. All rights reserved.

Confidentiality Status

This document is **NOT OPEN ACCESS**. The distribution is restricted to certified company.

This document is **CONFIDENTIAL**.

Feedback on this document

If you have any comments on this document, please contact your channel to our company.

Shmt Web address

<http://www.shmt.com>

Confidential

Contents

1. INTRODUCTION	7
2. Reference Application.....	8
2.1. Power On/Off Sequence	8
2.2. PLL Application	9
2.3. DDR Application	11
2.4. ARM ICE Application	13
2.4.1. Signals.....	13
2.4.2. Schematic	13
2.5. USB Application	15
2.5.1. Board Application	15
2.5.2. PCB Layout.....	16
2.6. DAC Application	18
2.6.1. Overview	18
2.6.2. Block diagram	19
2.6.3. Operation	20
2.6.4. PCB guidelines	22

Figures

Figure 3- 1 Power On/Off Sequence	8
Figure 3- 2 PLL Connection Diagram	9
Figure 3- 3 Tank Circuit for the Fundamental Mode Oscillation	9
Figure 3- 5 SSTL2 POC signal waveforms	11
Figure 3- 6 SSTL2 Class I termination configuration	12
Figure 3- 7 MultiICE pin connections	13
Figure 3- 8 PCB Schematic	15
Figure 3- 9 PCB Layout for USB 2.0 signal lines.....	16
Figure 3- 10 Space of USB 2.0 signal lines.....	16
Figure 3- 11 Component to USB 2.0 signal lines.....	17
Figure 3- 12 USB 2.0 signal and ground plane.....	17
Figure 3- 13 USB Crystal	17
Figure 3- 14 Video DAC Diagram	19
Figure 3- 15 mode1/2 iref connection.....	20
Figure 3- 16 mode4 iref connection.....	21
Figure 3- 17 power supply decoupling.....	22
Figure 3- 18 simple configuration to implement output to voltage conversion..	23
Figure 3- 19 34mA output configuration to convert current to voltage (Normal)	23
Figure 3- 20 17mA output configuration to convert current to voltage.....	24
Figure 3- 21 Reference guideline.....	24

Tables

Table 3- 1 PLL Power Description	9
Table 3- 2 Pin Name of SSTL2 Power and Ground Cells	11
Table 3- 3 MultiICE signals	13
Table 3- 4 USB Pin Name Mapping.....	15
Table 3- 5 Operation mode	20

Confidential

1. INTRODUCTION

본 문서는 CT-500 의 Board reference application과 (주)상화마이크로텍에서 제공하는 CT500 SOC의 PCB application에 대한 내용을 다룬다.

Confidential

2. Reference Application

2.1. Power On / Off Sequence

CT500 has multiple power domains as following:

- IO Power domains
 - SSTL IO power domain(2.5V)
 - General IO Power domain(3.3V)
- Core Power domains(1.2V)
- PLL Power domain(1.2V)


Power-Up Sequence

The power up sequence **MUST** be in the order of turning on higher voltage first, then turning on core voltage afterwards.

Power-Down Sequence

The POC circuit is only functional during the power-up sequence, and would not work during the power-down sequence. However, to save the transient current that consumes power, the lower voltage (VDD) should be powered down first and then the higher one (VDDPST).

Figure 3- 1 Power On/Off Sequence

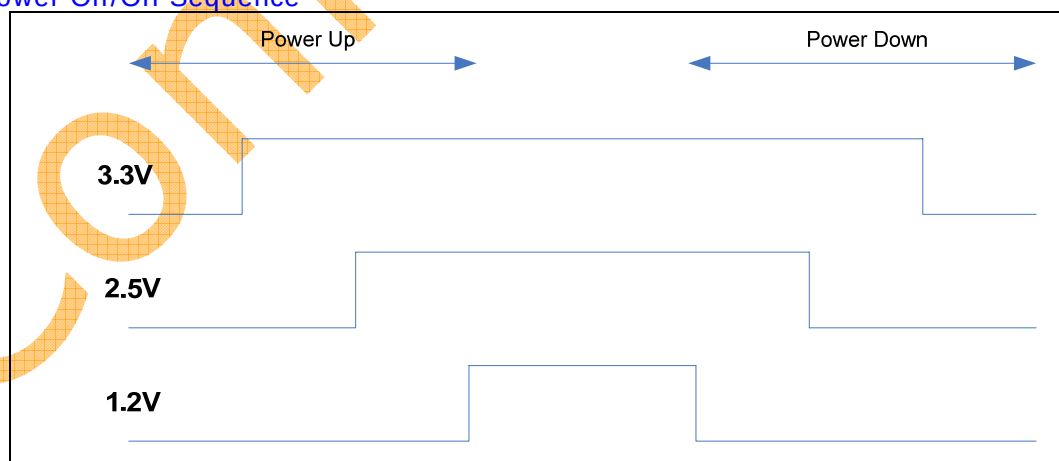

2.2. PLL Application

Table 3- 1 PLL Power Description

PLL_DVSS	power	PLL Dedicated Digital ground
PLL_DVDD	power	PLL Dedicated Digital power supply +1.2V
PLL_IOVSS	power	PLL IO ground
PLL_IOVDD	power	PLL 1.2V IO Power
PLL_AVSS	power	PLL Dedicated Analog ground
PLL_AVDD	power	PLL Dedicated Analog power supply +1.2V

Figure 3- 2 PLL Connection Diagram


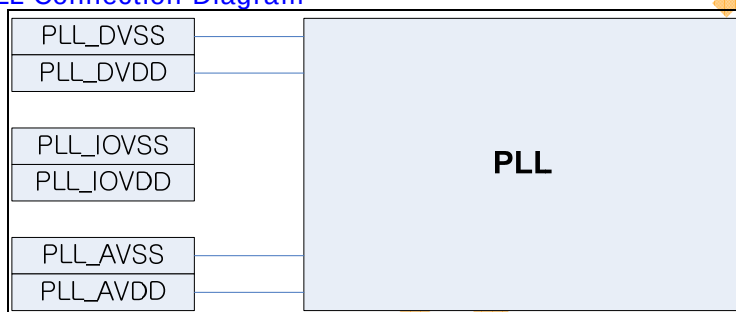


Figure 3- 3 Tank Circuit for the Fundamental Mode Oscillation

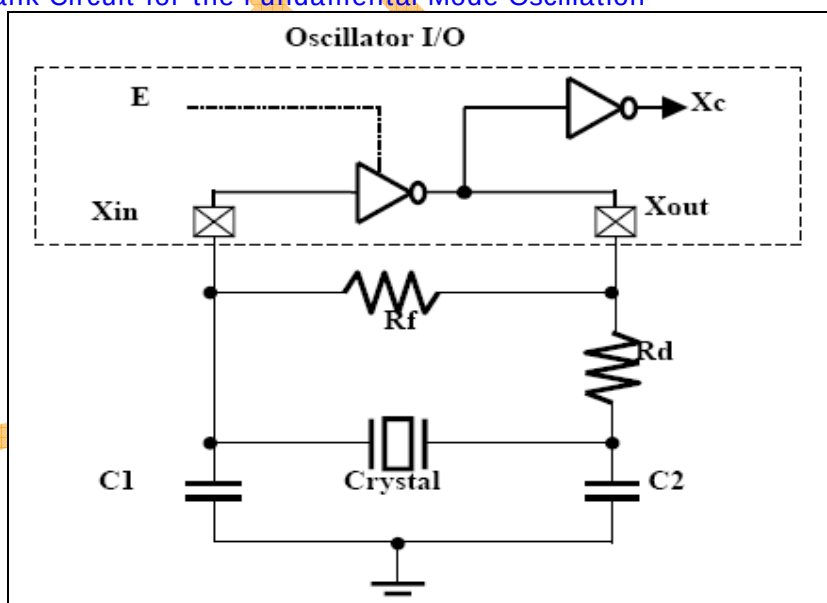

CL = 8pF

Maximum ESR = 40 ohm

Figure 3-1 shows several components that decide the behavior of oscillation, and they affect the loop in many aspects:

- R_f represents the feedback resistor to bias the inverter in the high gain region. R_f cannot be too low, or the loop may fail to oscillate. Normally, an R_f of 1M Ω is sufficient for MHz band applications.

- R_d represents the damping resistor that helps increase stability, save power, and suppress the gain in the high frequency area. The trade-off for inserting R_d is the reduction of negative resistance. Therefore, R_d cannot be too large, or the loop could fail to oscillate. Sometimes users may drop R_d in high frequency applications to reduce production costs.

- C_1 and C_2 are decided according to the crystal or resonator CL specification. In the steady state of oscillating, CL is defined as $(C_1 \times C_2)/(C_1 + C_2)$. In fact, the I/O ports, the bond pad, and package pin all contribute the parasitic capacitance to C_1 and C_2 . Therefore, we can rewrite CL to be $(C_1^* \times C_2^*)/(C_1^* + C_2^*)$, where $C_1^* = (C_1 + C_{in, stray})$ and $C_2^* = (C_2 + C_{out, stray})$. In this example, the required C_1 and C_2 would be reduced.

2.3. DDR Application


Table 3- 2 Pin Name of SSTL2 Power and Ground Cells

Cell Name	Descriptions	Pin Name
PVDDSSSTL	SSTL2 power pad (1.2V) for pre-driver and core logic	VDDSSSTL / VDDC
PVSSSSSTL	SSTL2 ground pad pre-driver and core logic	VSSSSSTL / VSSC
PVDDPSSTL	SSTL2 power pad (2.5V) for post-driver	VDDPSSTL
PVSSPSSTL	SSTL2 ground pad for post-driver	VSSPSSTL
PVREFSSTL	SSTL2 power pad for receiver reference voltage (1.25V) *	VREFSSTL
PVSSRSSTL	SSTL2 ground pad for VREFSSTL signal shielding	VSSRSSTL
PVD25SSTL	SSTL2 power pad (2.5V) for level shifter	VD25SSTL

V_{REF} on board or VREFSSTL in the chip are both sensitive to coupling noise.

On the board, it's suggested to provide the V_{DDQ}/V_{SS} traces shielding to the V_{REF} trace in parallel.

Figure 3- 4 SSTL2 POC signal waveforms

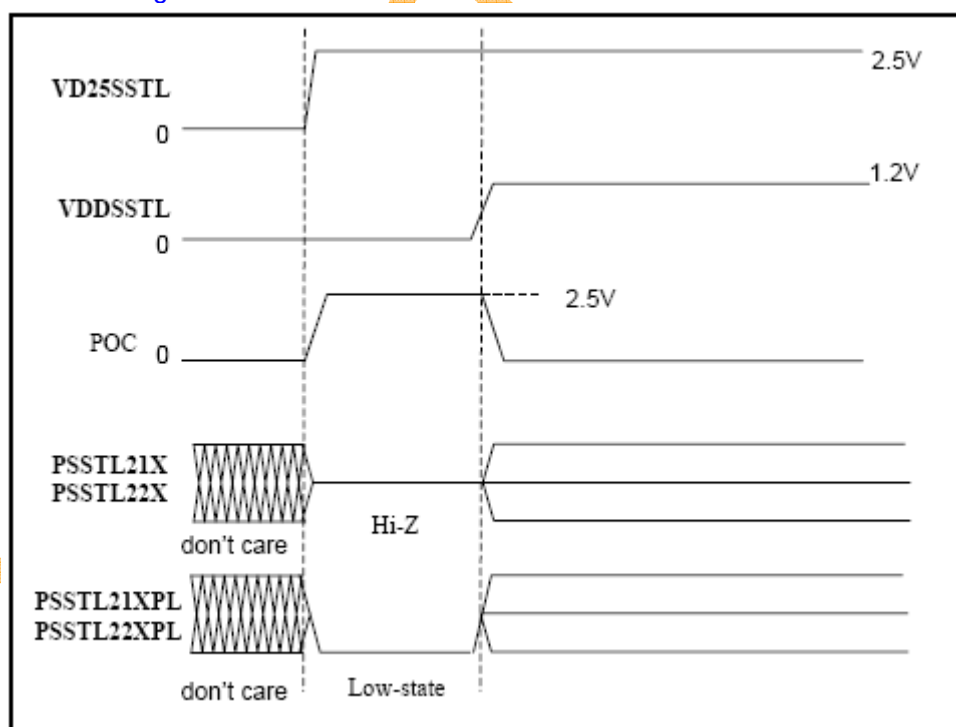


The POC circuit is located inside the **PVD25POCSSTL** cell. This **PVD25POCSSTL** cell has the same role as the **PVD25SSTL** cell (to provide "high" voltage to the I/O

ring). The POC detects a power-on condition and derives a signal (also named POC) for distribution to the rest of the I/Os **Power-up Sequence**

To avoid any damage on the ESD device during power-on, user must obey the TSMC's power-up sequence as defined in standard library application notes. 2.5V power for both **PVDDPSSTL** and **PVD25SSTL** need to be turned on before the other power voltages. 1.2V power supply for **PVDDSSSTL** and 1.25V for **PVREFSSTL** must be on once 2.5V power supplies are fully turned on

Figure 3- 5 SSTL2 Class I termination configuration

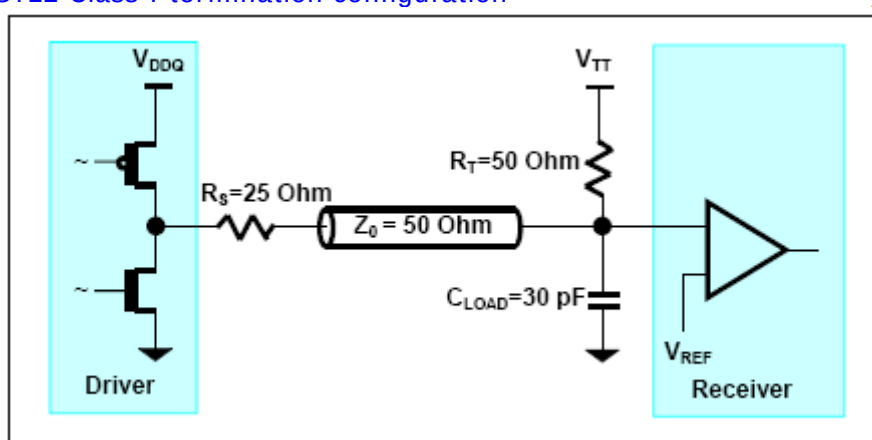


SSTL2 Class I transceiver is suitable for point-to-point application that has the transmission line characteristic impedance (Z_0) to be 50 Ohm. To reduce the reflection of the transmission line effect, the parallel termination resistor (R_T) should match to the line characteristic impedance, which is also 50 Ohm. The configuration of the connection from driver to receiver and its termination is shown in Figure3-3.

2.4. ARM ICE Application

MultiICE pin connections

Figure 3- 6 MultiICE pin connections

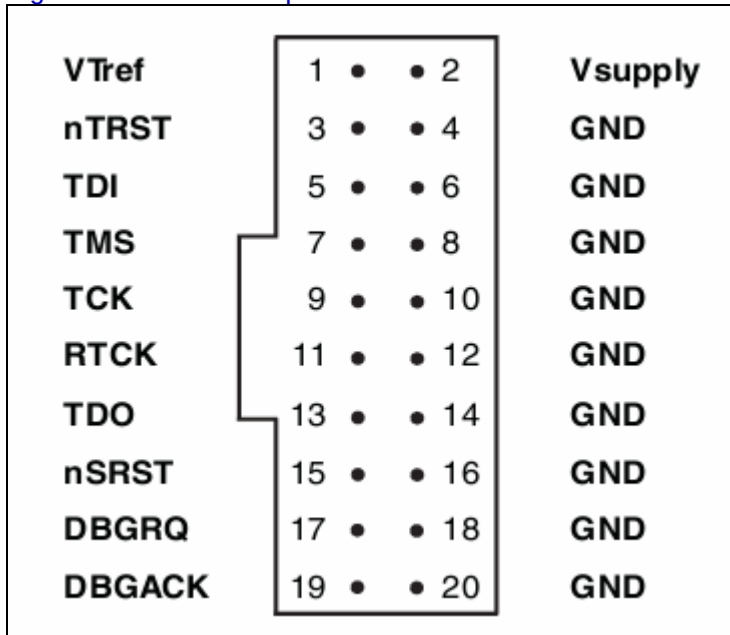


2.4.1. Signals

Table 3- 3 MultiICE signals

Signal Name	I / O	Description
VTref	I	Target reference voltage. RTCK와 TDO의 logic-level의 기준 전압을 알려준다.
Vsupply	I	MultiICE의 target보드쪽에서의 공급 전원.
(ARMICE_)nTRST	O	JTAG reset
(ARMICE_)TDI	O	JTAG data output to target cpu
(ARMICE_)TMS	O	JTAG test mode signal
(ARMICE_)TCK	O	JTAG JTAG test clock
(ARMICE_)RTCK	I	Return test clock
(ARMICE_)TDO	I	JTAG data input from target cpu
(ARMICE_)nSRST	I/O	All system is reset. 이 신호는 option으로 사용비중은 높으나 필수 신호는 아니다.
DBGRQ	O	Debug request. Not used in the MultiICE.
DBGACK	I	Debug acknowledge. Not used in the MultiICE.

2.4.2. Schematic

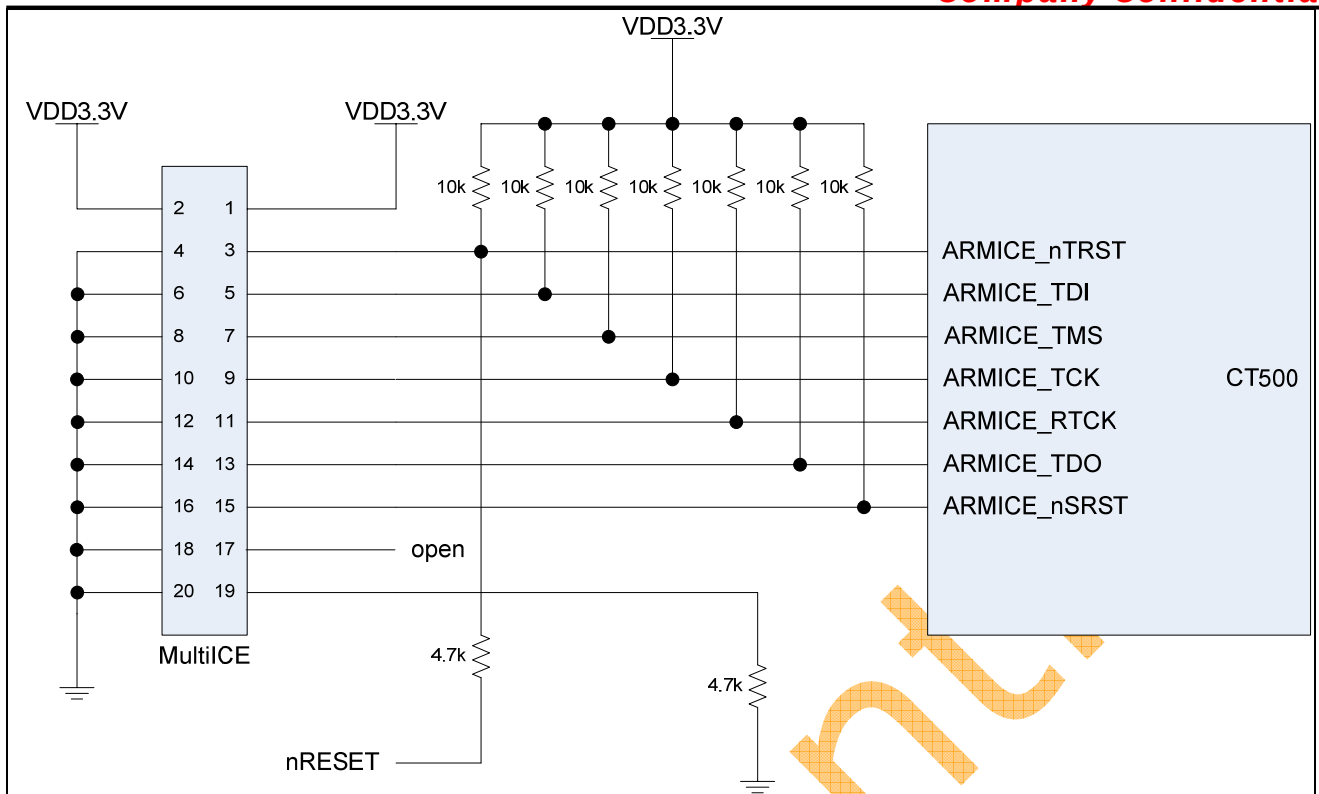


- CT500의 IO전압이 3.3V이므로 Vsupply와 VTref에 3.3V를 공급한다.
- nRESET은 system reset으로 CT500이 reset될 때 JTAG control block도 reset시킨다.

DBGREQ와 DBACK는 ARM MultiICE에서는 사용하지 않으므로 입력신호만 pulldown시킨다.

2.5. USB Application

2.5.1. Board Application

Figure 3- 7 PCB Schematic

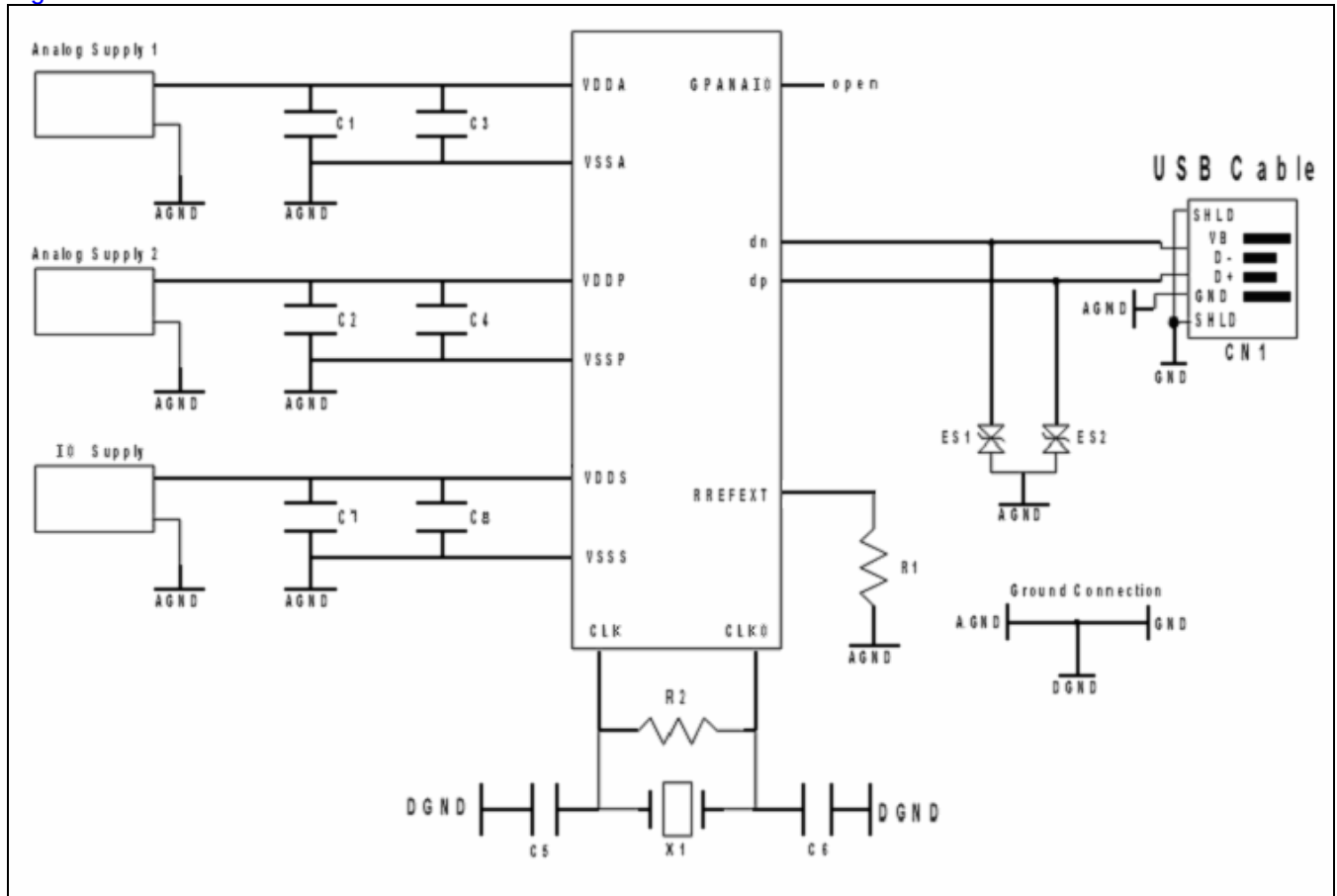

Analog Supply 1 : 3.3V
 Analog Supply 2 : 1.2V
 IO Supply : 3.3V
 R1(reference resistor) : 6.04kohm 오차 1%
 X1 : 24Mhz
 C5, C6 : 22pF
 R2 : 1Mohm
 C1, C2, C7 : 100nF
 C3, C4, C8 : 1nF

Table 3- 4 USB Pin Name Mapping


Pin Name	Schematic Name	Description
USB_vdda	VDDA	USB PHY Analog core 3.3V
USB_vdds	VDDS	USB PHY IO ring power 3.3V
USB_DN	dn	Negative output channel that is connected to the serial USB cable
USB_DP	dp	Positive output channel that is connected to the serial USB cable
USB_vssa	VSSA	USB PHY Analog core ground

USB_vsss	VSSS	USB PHY IO ring ground
USB_rrefext	RREFEXT	USB PHY External resistor connection for current reference
USB_gpanaio	GPANAIO	USB PHY Test Pins for Observability of Internal Analog Signals
USB_vddp	VDDP	USB PLL 1.2V
USB_vssp	VSSP	USB PLL ground

2.5.2. PCB Layout


USB 2.0 data signal line은 parallel하게 배치 해야 하며 그 간격을 일정하게 유지해야 한다. 각 line의 impedance는 45ohm, 두 line간의 impedance는 90ohm을 이루도록 해야 한다.

Figure 3- 8 PCB Layout for USB 2.0 signal lines

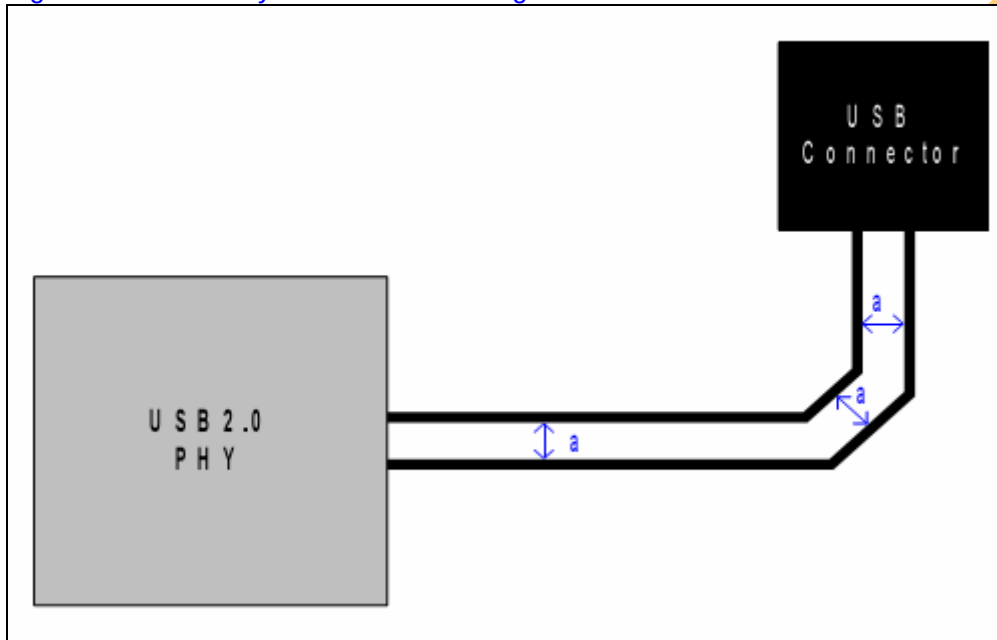

USB signal과 다른 signal과 crosstalk을 최소화 하기 위하여 다음 Figure와 같이 간격을 두어야 한다.


Figure 3- 9 Space of USB 2.0 signal lines

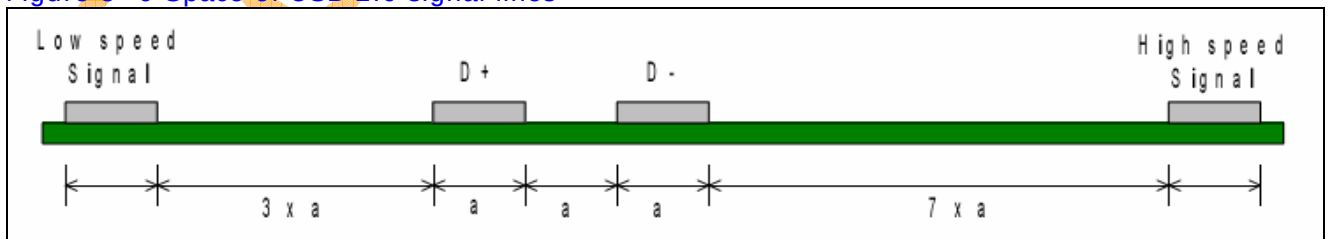

USB 2.0 PHY와 connector간의 거리는 457mm 이내가 되어야 한다.


USB 2.0 data line에 resistor를 연결할 때에는 stub이 발생하지 않게 하기 위해서 아래 Figure와 같이 연결한다.

Figure 3- 10 Component to USB 2.0 signal lines

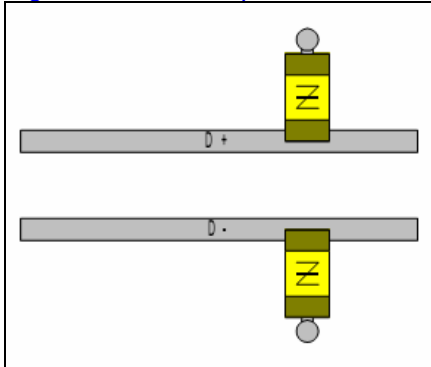


USB 2.0 data line을 ground plane으로 감쌀 경우에는 하나의 plane으로 해야 하며 여러 개의 Plane으로 나뉘어지면 안 된다.

Figure 3- 11 USB 2.0 signal and ground plane

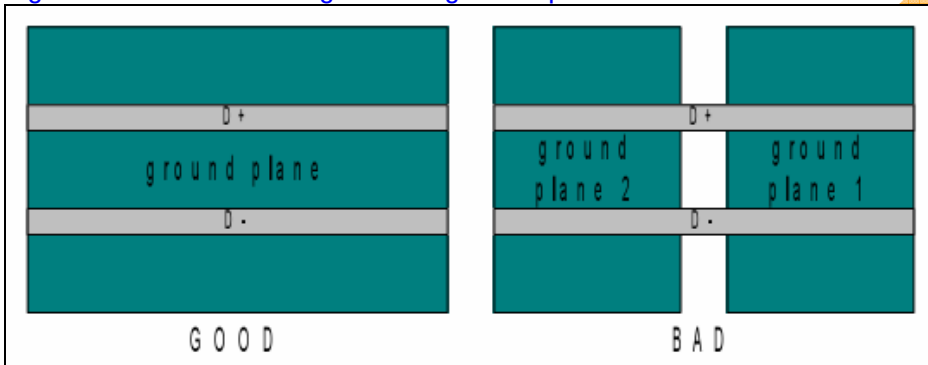

Crystal은 다음 Figure와 같이 ground plane으로 주위를 감싼다.

Figure 3- 12 USB Crystal

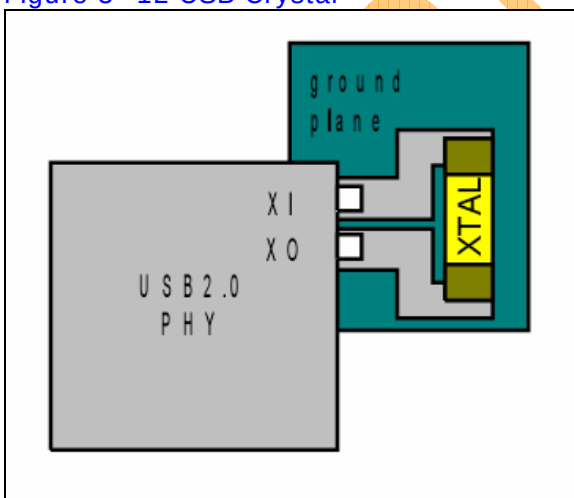

2.6. DAC Application

2.6.1. Overview

This is 10-bit single Video DAC. The circuit is a current output DAC designed to be loaded by double terminated 75 Ohm lines


(1) Feature

- 10bit Resolution
- 27Mhz Update Rate
- Full-scale Output Currents : 17/34mA
- 2.43V to 3.6V Analog Power Supply
- 1.08V to 1.32V Digital Power Supply

Confidential

2.6.2. Block diagram

Figure 3- 13 Video DAC Diagram

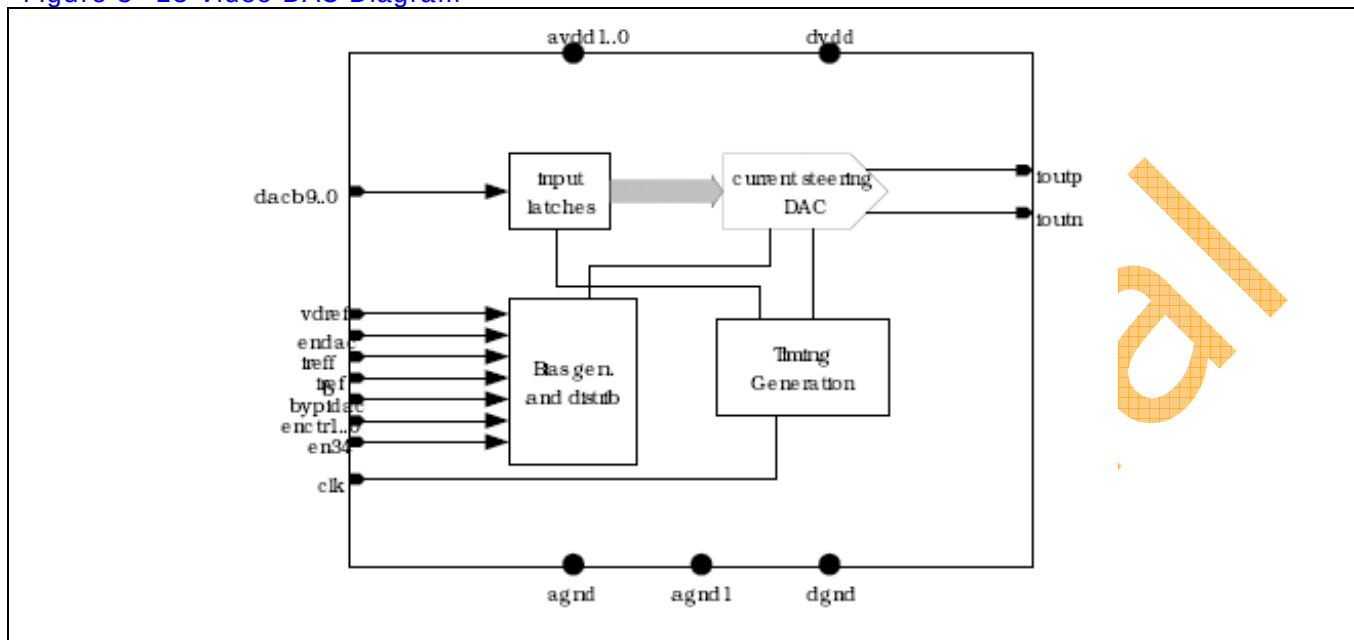

2.6.3. Operation

(1) Operation mode setting

Table 3- 5 Operation mode

Mode	Description	Configuration		
		EN_DAC0	EN_DAC0_34	BYPIDAC
0	Complete Power Down	0	X	X
1	Normal mode, 17mA output full scale mode	1	0	0
2	Normal mode, 34mA output full scale mode	1	1	0
3	DAC is active	1	X	0
4	DAC active, using external reference currents	1	X	1

기본적으로 External Bias mode 와 Internal Bias mode로 구분됩니다. 각 설정 register는 Video Encoder (Video Encoder Control reg.)를 통하여 설정 할 수 있습니다.


(2) mode 0

모든 전원을 차단한 상태 입니다. EN_DAC0 를 'LOW' 설정함으로써 다른 설정에 관계없이 Power-Down mode로 설정 됩니다.

(3) mode 1 / 2

Internal Bias mode를 사용하며, mode1 에 경우에는 17mA로 출력 전류를 구동합니다. 출력 전류 선택은 EN_DAC_34 를 통하여 설정할 수 있습니다. (Rref :: 1150 Ohm)


Figure 3- 14 mode1/2 iref connection

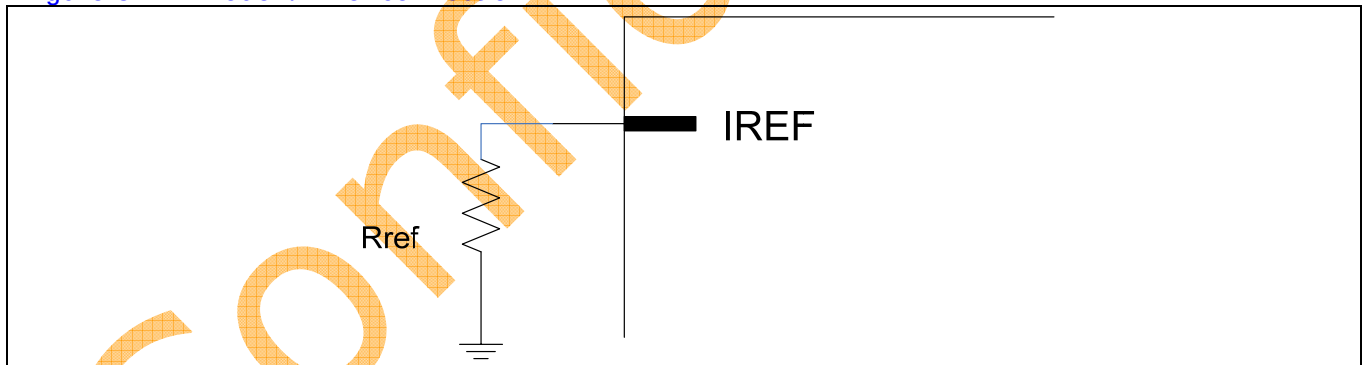

(4) mode 4

External Bias mode를 사용하는 경우 입니다.

Figure 3- 15 mode4 iref connection

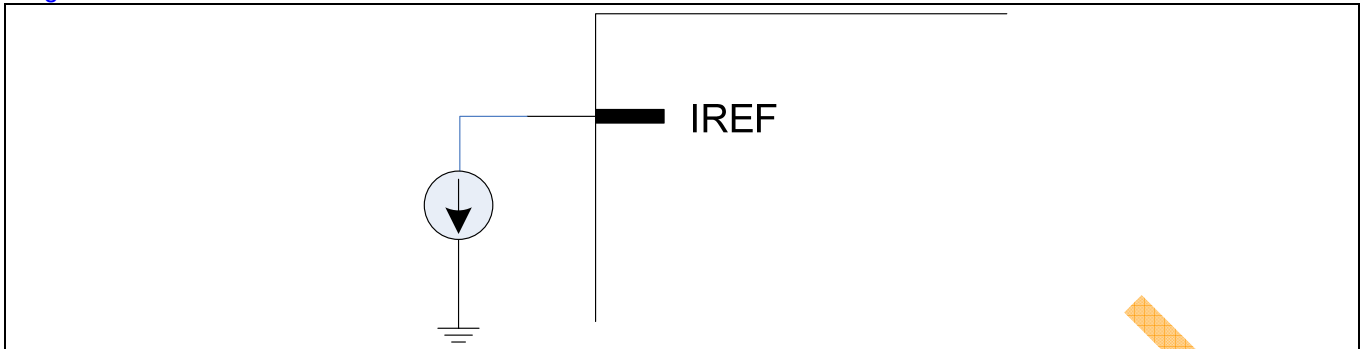


Confidential

2.6.4. PCB guidelines

(1) Power supply decoupling


Figure 3- 16 power supply decoupling

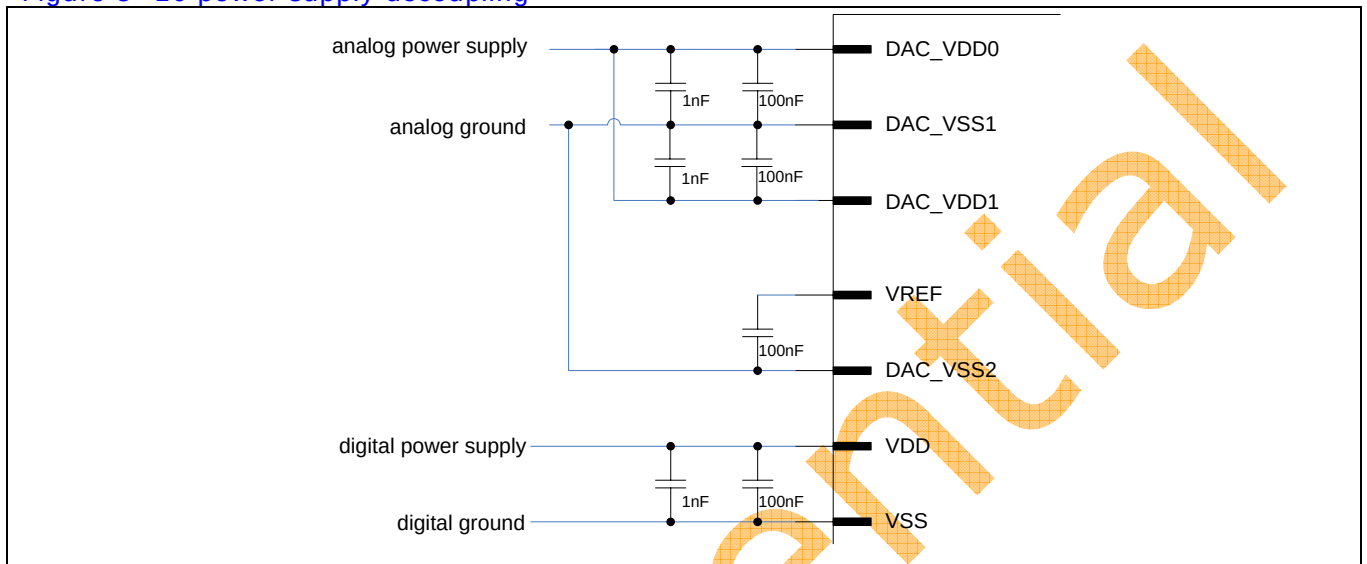

100nF cap은 가능한 칩에 가까이 위치하고, 특성이 좋은 소자를 사용합니다.


(2) Analog output configuration

Figure 3- 17 simple configuration to implement output to voltage conversion

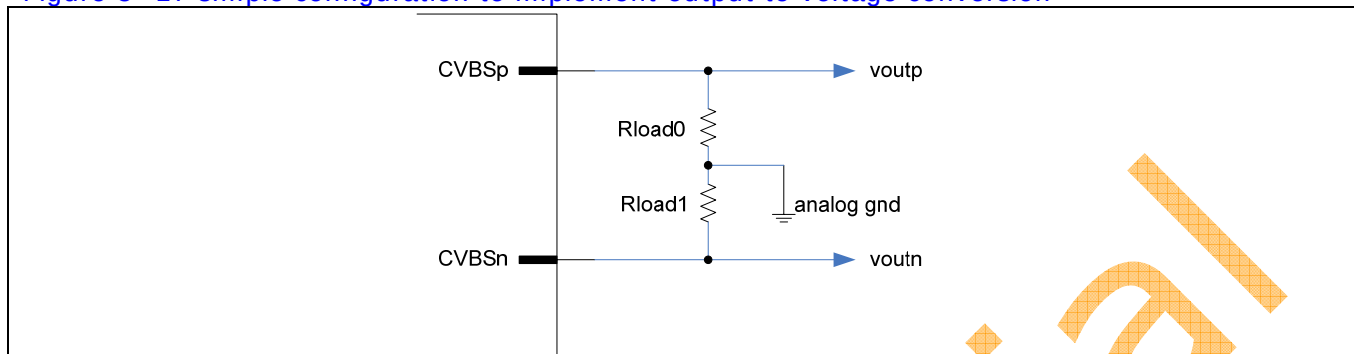


전압 출력에 간단한 예 입니다. 저항 값은 출력되는 전압 폭을 고려하여 설정합니다.
34mA(EN_DAC0_34 = 'High') 전류 폭을 갖도록 설정 할 경우 Rload0/Rload1 이 37.5 Ohm이면
±1.275V 폭을 갖게 됩니다.

Figure 3- 18 34mA output configuration to convert current to voltage (Normal)

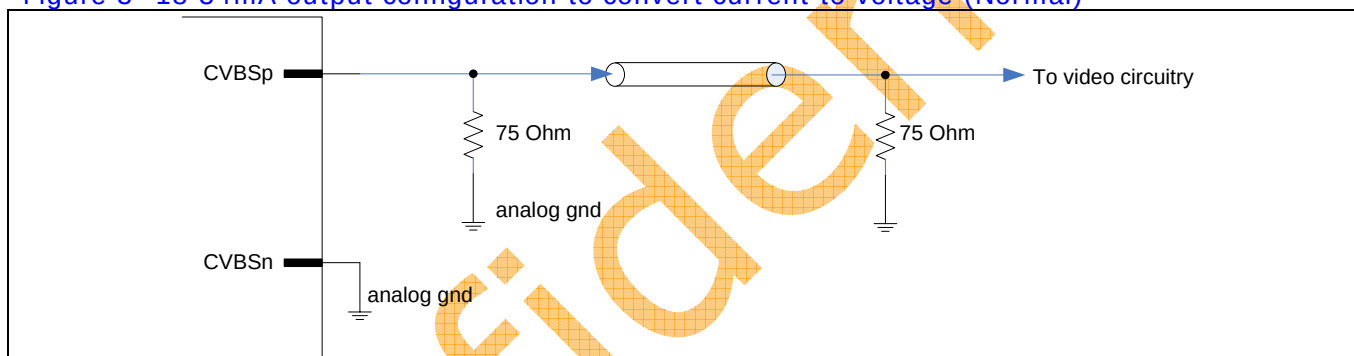


가장 일반적인 경우에 Video output 출력을 보여 줍니다. 종단 저항은 37.5 Ohm 인 경우이며, EN DAC0 34 = 'High' 설정하였을 경우입니다. 위와 같은 경우에 출력 전압 폭은 1.275V 가 됩니다.

Figure 3- 19 17mA output configuration to convert current to voltage

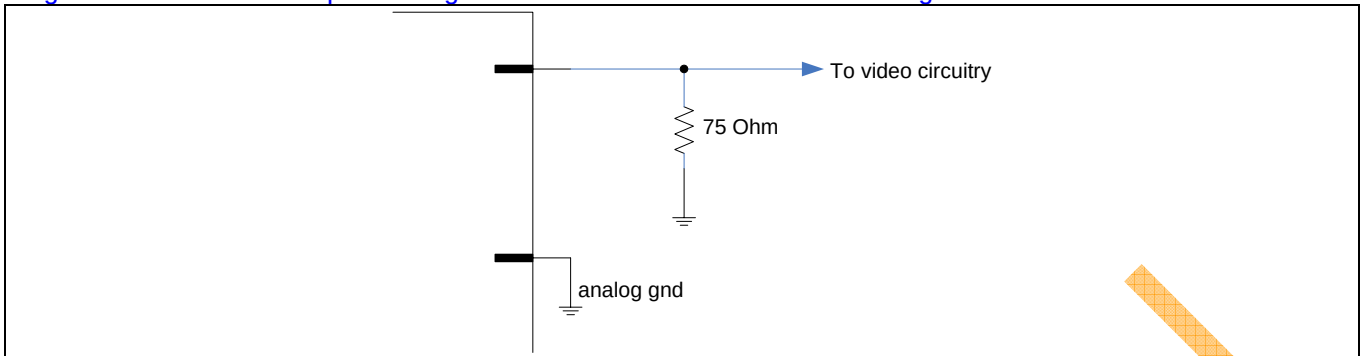

EN_DAC0_34 = 'Low' 설정하였을 경우 입니다. 출력 전류 폭이 17mA로 설정되고 전압 폭은 1.275V 입니다.

Figure 3- 20 Reference guideline

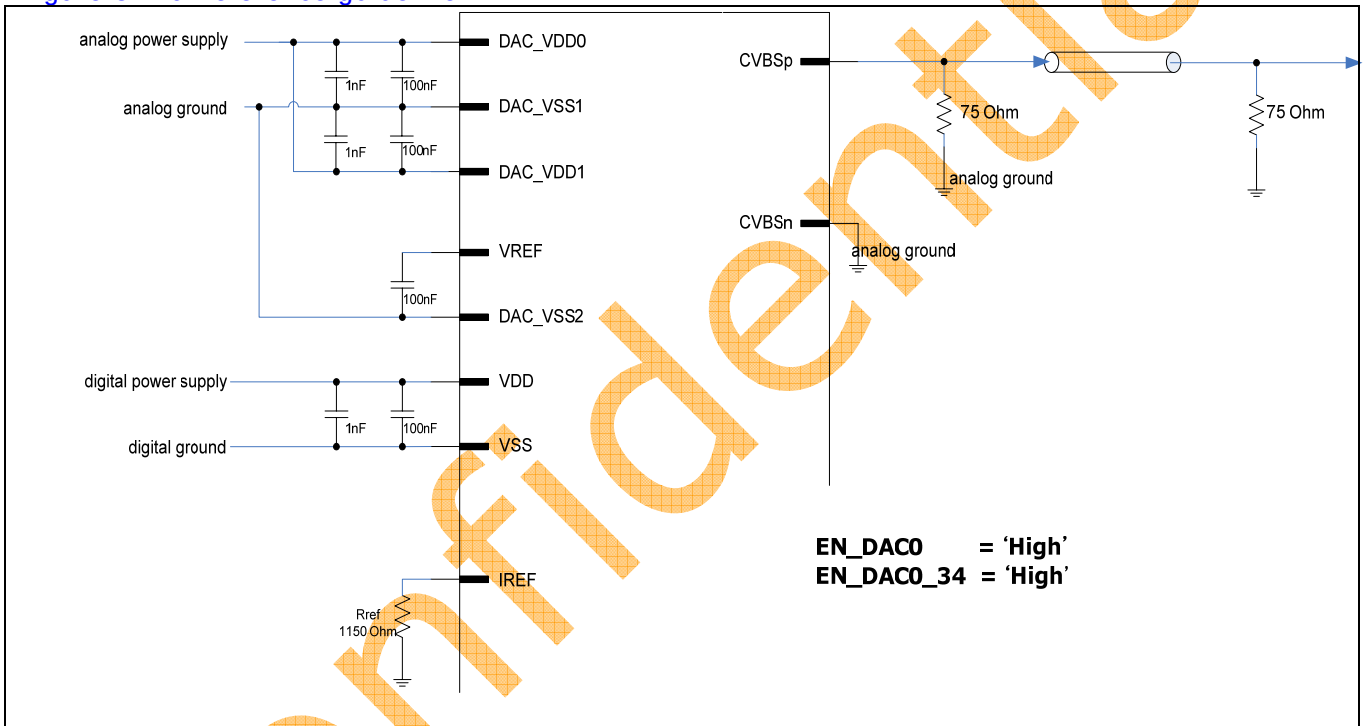

34mA 출력 전류 폭을 갖는 것을 기본으로 하며 Rref 는 1150 Ohm을 사용합니다.